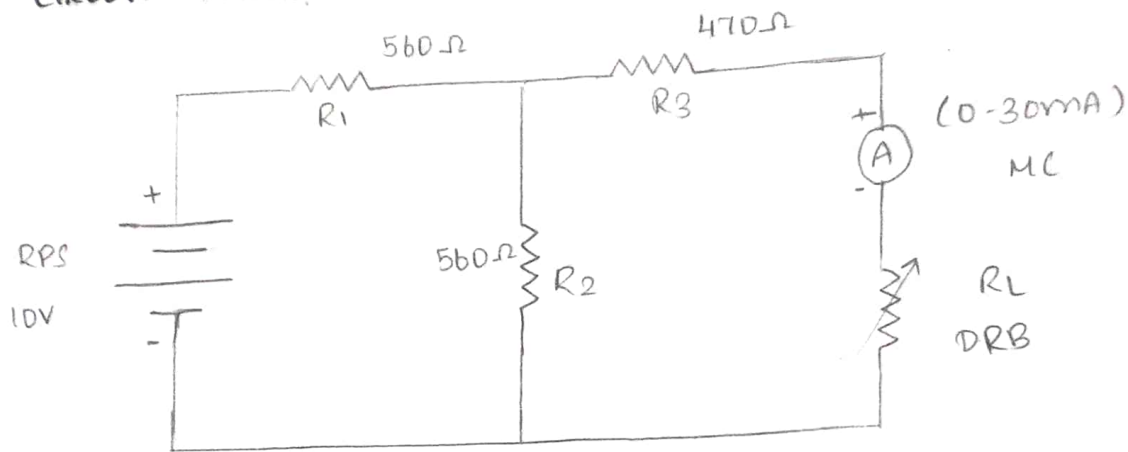


# CIRCUIT DIAGRAM:



## MODEL GRAPH:-

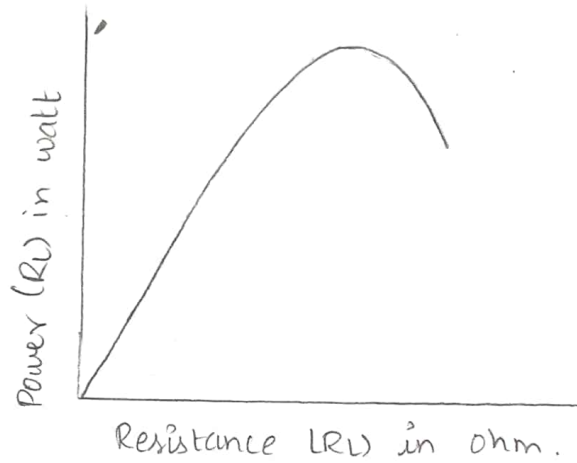


TABLE : FOR PRACTICAL CALCULATION :-

S.No	Load resistance ( $R_L$ )	Load current ( $I_L$ ) in amps.	Load voltage ( $V_L$ ) in volts.	Load power ( $P_L$ ) in watts.
1	1KΩ	2.96mA	2.96V	8.76mW
2	150KΩ	5.53mA	0.995V	6.60mW
3	100KΩ	6.00mA	0.6V	3.6mW
4	470KΩ	4.13mA	1.94V	8.01mW
5	5KΩ	0.85mA	4.335V	3.68mW

## VERIFICATION OF MAXIMUM POWER TRANSFER THEOREM.

AIM:

To measure the power absorbed in load and to verify that the power absorbed in a load is maximum only when load resistance is equal to the source resistance.

APPARATUS REQUIRED:

S.No	NAME OF THE APPARATUS	SPECIFICATION	QUANTITY
1.	Voltmeter	(0-15 V) MC	1
2.	Ammeter	(0-500 mA) MC	1
3.	Resistors.	560 $\Omega$ , 470 $\Omega$	2 1
4.	RPS (DC supply)	15 V	1

PROCEDURE:

1. Make connection as per the circuit diagram.
2. Change the resistors  $R_L$  whose value close to  $R_{Th}$ , measure the corresponding  $V_L$ ,  $I_L$  and calculate  $P_L$  and enter into the table (2).
3. Plot a graph between  $R_L$  and  $P_L$  and find the  $R_L$  corresponding to maximum power transfer.
4. Verify the measured values of  $R_L$  at maximum power transfer as same as calculated and found graphically.

CALCULATION :

$$V_{th} = \frac{V \times R_2}{R_1 + R_2} = \frac{10 \times 560}{560 + 560} = 5V$$

$$R_{th} = \frac{560 \times 560}{2(560)} + 470 = 280 + 470 = 750 \Omega$$

$$R_L = R_{th}$$

$$P_L = \frac{(V_{th})^2}{4(R_{th})} = \frac{5^2}{4 \times 750} = \frac{25}{4 \times 750} = \frac{25}{3000}$$

$$= 8.33 \text{ mW}$$

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{5}{1500} = 0.00333 \text{ A}$$

$$I_L = 3.33 \text{ mA}$$

$$V_L = I_L \times R_L = 3.33 \times 10^{-3} \times 750$$

$$V_L = 2.5V$$

RESULT:

Thus maximum power transfer theorem is verified practically and theoretically.